

ELECENG 2CJ4 Lab 4

Raeed Hassan
hassam41

L01
McMaster University
October 26, 2020

- a) The measured values for V_{sat+} and V_{sat-} are $V_{sat+} = 7.1378$ and $V_{sat-} = -7.13792$. The calculated values for V_{th+} and V_{th-} are $V_{th+} = \frac{R_2}{R_1+R_2} V_{sat+} = 7.1378 \left(\frac{10k}{35k} \right) = 2.039V$ and $V_{th-} = \frac{R_2}{R_1+R_2} V_{sat-} = -7.13792 \left(\frac{10k}{35k} \right) = -2.039V$.
- b) The waveforms for $v_c(t)$ and $v_{out}(t)$ for $C = 10nF$, $R_3 = 100k\Omega$ can be seen in Figure 1. The period was measured to be approximately $500\mu s$ (2 kHz). The theoretical period was calculated to be $T = RC \left(\ln \frac{V_{sat+}-V_{th-}}{V_{sat+}-V_{th+}} + \ln \frac{V_{sat-}-V_{th+}}{V_{sat-}-V_{th-}} \right) = 0.001175 \approx 1175\mu s$ (851 Hz). The calculated theoretical value was over double the measured period.

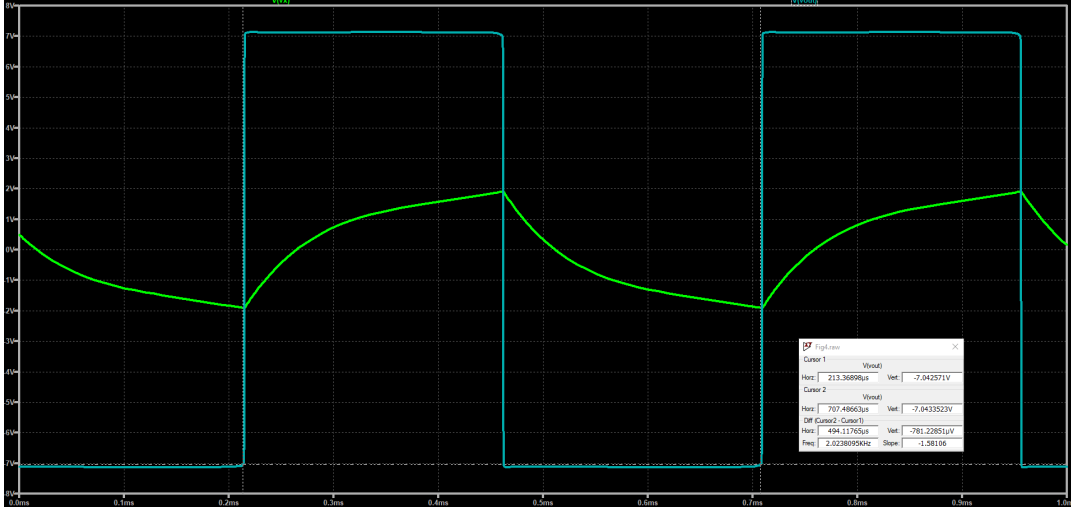


Figure 1: $v_c(t)$ (green) and $v_{out}(t)$ (cyan) for $C = 10nF$, $R_3 = 100k\Omega$

- c) The waveforms for $v_c(t)$ and $v_{out}(t)$ for $C = 10nF$, $R_3 = 10k\Omega$ can be seen in Figure 2. The period was measured to be approximately $94\mu s$ (10.7 kHz).

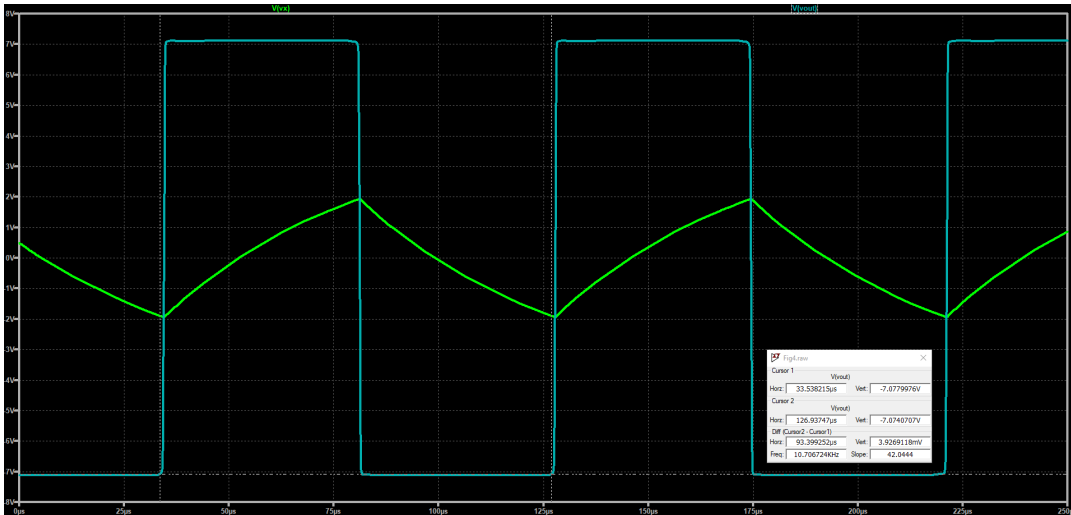


Figure 2: $v_c(t)$ (green) and $v_{out}(t)$ (cyan) for $C = 10nF$, $R_3 = 10k\Omega$

The waveforms for $v_c(t)$ and $v_{out}(t)$ for $C = 100nF$, $R_3 = 100k\Omega$ can be seen in Figure 3. The period was measured to be approximately 5ms (200 Hz).

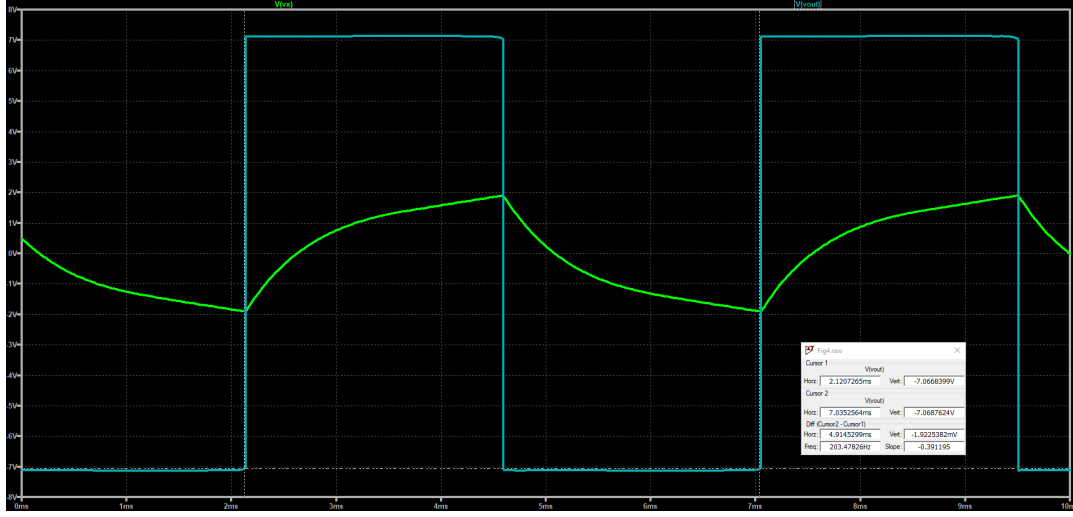


Figure 3: $v_c(t)$ (green) and $v_{out}(t)$ (cyan) for $C = 100nF$, $R_3 = 100k\Omega$

The waveforms for $v_c(t)$ and $v_{out}(t)$ for $C = 100nF$, $R_3 = 10k\Omega$ can be seen in Figure 4. The period was measured to be approximately $915\mu s$ (1.09 kHz).

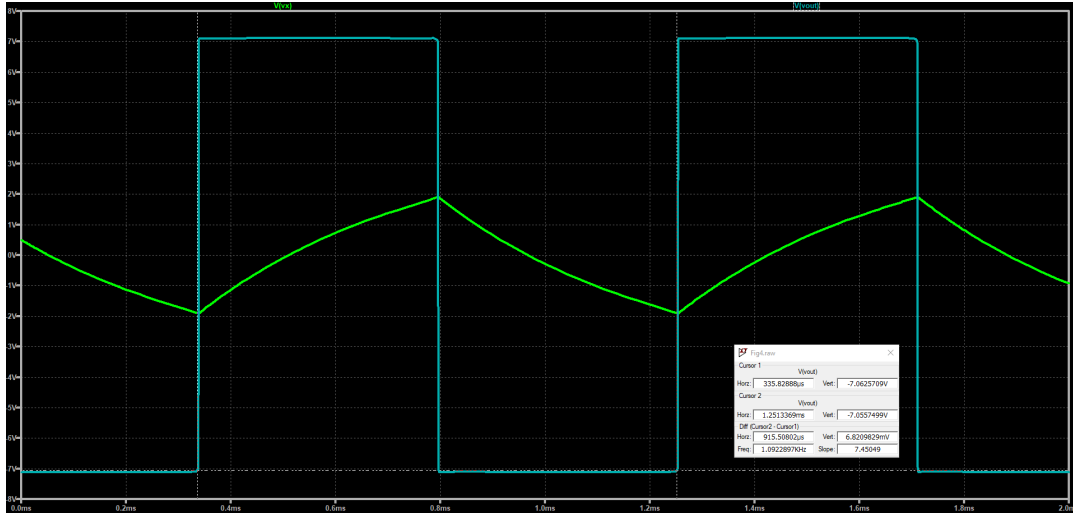


Figure 4: $v_c(t)$ (green) and $v_{out}(t)$ (cyan) for $C = 100nF$, $R_3 = 10k\Omega$

- d) The waveforms for $v_c(t)$ and $v_{out}(t)$ can be seen in Figure 5. The period was measured to be approximately $310\mu s$ (3.22 KHz).

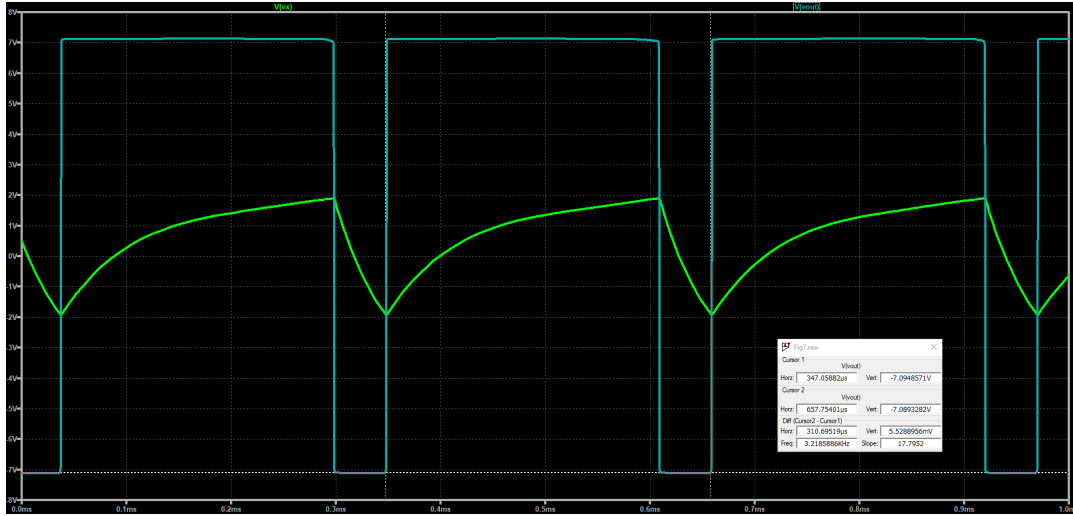


Figure 5: $v_c(t)$ (green) and $v_{out}(t)$ (cyan)